

2 A multimeter having a sensitivity of  $2000 \text{ A/V}$  is used for a measurement of voltage across a CRT having an o/p resistance of  $10 \text{ k}\Omega$ .


The open circuit voltage of a CRT is 6V

- (a) Find the reading of m.m. when it is set to its 10V range / scale.
- (b) Find the % error if the o/p R of the CRT is  $1000\Omega$  & open circuit voltage is 6V at its 10V scale.
- (c) Find % error
- (d) comment on your result

3. A 50V range voltmeter is connected across the terminal A & B of a CRT below.

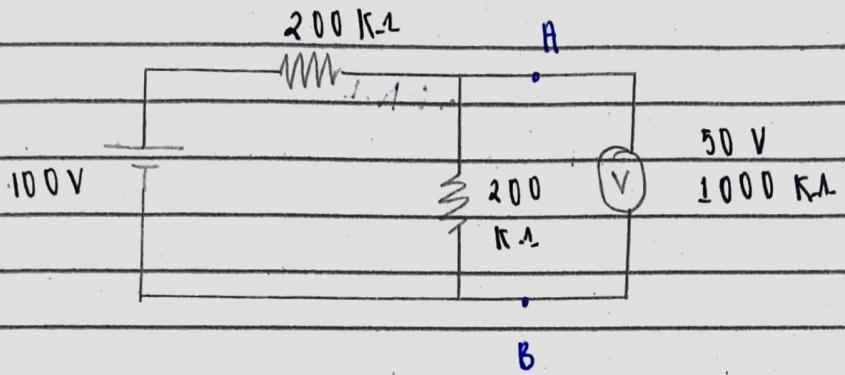- (a) Find reading of voltmeter under open circuit & loaded condn
- (b) Find accuracy & loading error  
(% error)

Voltmeter has a resistance ( $R$ ) of  $1000 \text{ k}\Omega$



10<sup>th</sup>  
Dec

③ ~~SQIN~~

Given,

$$\text{sensitivity } (S) = 2000 \text{ }\Omega/\text{V}$$

$$\text{open circuit voltage} = 6\text{V}$$

$$\text{load resistance of meter} = 10 \text{ k}\Omega$$


$$\cdot \text{range of voltmeter} = 10 \text{ V}$$




Total internal resistance ( $R_i$ )

$$= 2000 * 10$$

$$= 20 \text{ k}\Omega$$

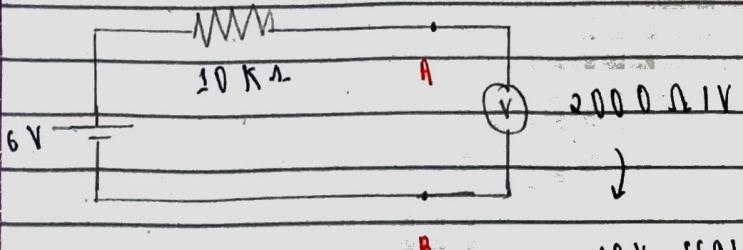

10V scale

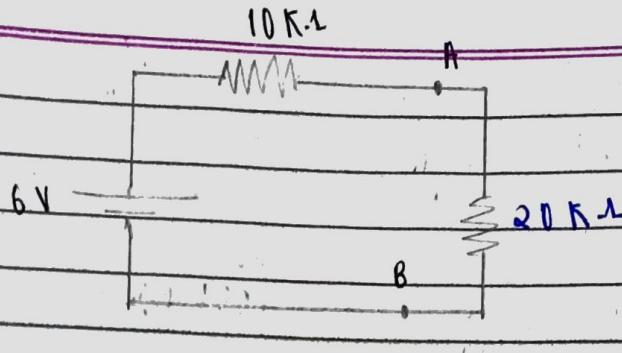

Now,

VOLTAGE ACROSS AB ( $V_{AB}$ )


$$= \frac{20}{10+20} * 6 \\ = 4V$$

Then,

% loading error

$$= \left| \frac{6-4}{6} \right| * 100 \\ = 33.33\%$$

2nd case

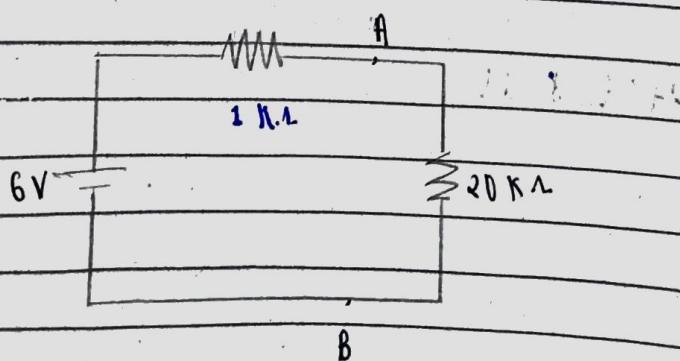

NOW,

VOLTAGE ACROSS AB (V<sub>AB</sub>)

$$= \frac{20}{1+20} * 6 \\ = 5.71 \text{ V}$$

Then,

$$\therefore \text{loading error} = \left| \frac{6 - 5.71}{6} \right| * 100 \\ = 4.76 \%$$


So,

when voltmeter having ilp resistance comparable to that of ckt are used for measurement purpose, it seriously modifies the value of test voltage.

When ilp impedance of source is quite  $\downarrow$  (low) as compared w. ilp impedance of voltmeter the error involved in measurement is quite small.

(3) SOLN


## a) OPEN CIRCUIT

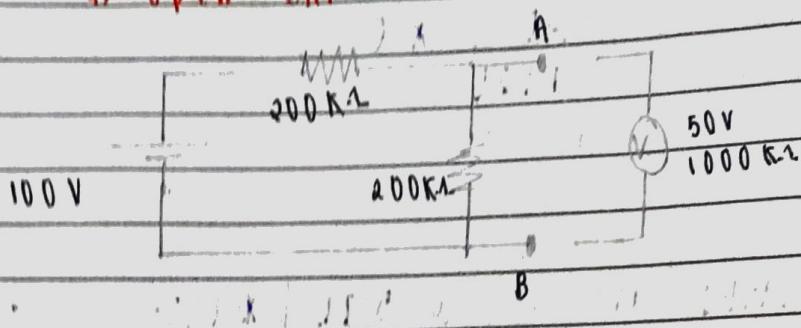

FOR this,

$$V_{AB} = \frac{200}{200+200} * 100 \\ = 50V$$

## 1000Ω COND

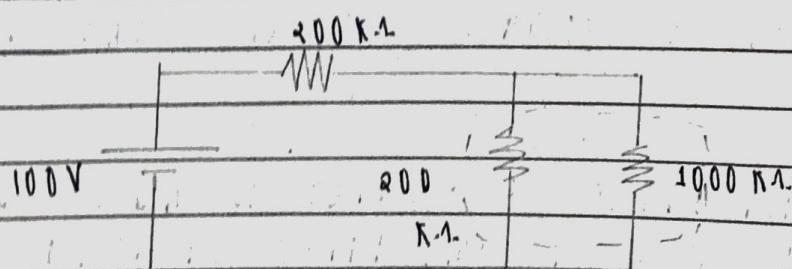

$$R = (200 // 1000) \\ = 500 \Omega$$

3

Voltage across AB,

$$V_{AB} = \frac{R}{R+200} * 100$$

$$= 45.45 V$$

1000 JODOH AVERAGE ERROR

∴ loading error ( $E_L$ )

$$= \left| \frac{50 - 45.45}{50} \right| * 100$$

$$= 9.1\%$$

ACTUAL AS OPEN Ckt M  
LOAD NEI

∴ ACCURACY

Y

$$100\% - E_L (\%)$$

$$= 100\% - 9.1\%$$

$$= 90.9\%$$

Q1. A bridge is balanced at 1000 Hz & has the following const.

ARM (AB) has  $0.2 \mu F$  pure capacitance

ARM (BC) has  $500 \Omega$  pure resistance

Q2. ARM (CD) has  $R = 300 \Omega$  in parallel  
 $\text{W.C} = 0.1 \mu F$ .

FIND:

value of R & C or I const. of arm CD

i) consider as series CRT

ii) consider as parallel CRT

Q2. A 1000 Hz bridge has following const.

ARM (AB) has  $R = 1000 \Omega$  in // W.  
capacitor  $C = 0.5 \mu F$

ARM (BC) has  $R = 1000 \Omega$  in series  
 $\text{W.C} = 0.5 \mu F$

Q3. ARM (CD) has  $R = 200 \Omega$  in series  
 $\text{W.L} = 30 \text{ mH}$

**FIND:**


the const: of arm DA to make the bridge balanced.

Express the result as pure resistor (R) in  $\parallel$  w.  
pure capacitor (C) or inductor (L)

ALSO,

express result as pure resistor (R) in series w.  
a pure capacitor (C) or inductor (L).

① *SOLN*

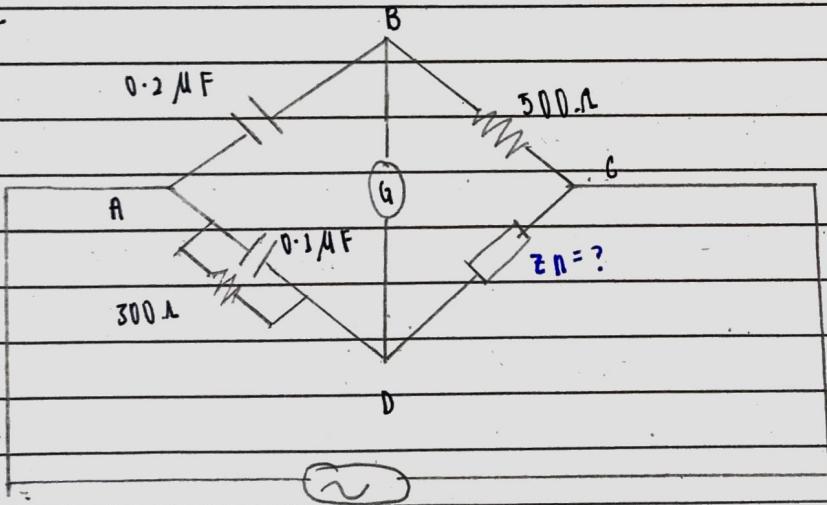

**•NOTE:**

$Z_n$  niko1000  $R + jX$  or  $\angle +ve$   
rayo vanc  
inductor ho

$R - jX$  or  $\angle -ve$  rayo vanc  
capacitor ho

$$\rightarrow R - j X_C$$

IN arm AB,

$$Z_{AB} = -j X_C$$

$$= \frac{-j}{wC} \rightarrow \frac{-j}{2\pi f C}$$

$$= \frac{-j}{2\pi \times 1000 \times 0.2 \times 10^{-6}}$$

$$= -j 795.77 \Omega$$

IN arm BC,

$$Z_{BC} = 500 \Omega$$


IN arm AD,

### • Note:



FOR II capacitor & R

$$-j X_C$$

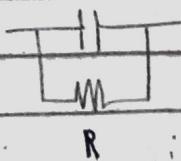

$$Z_{eq} = \frac{1}{R} + \frac{1}{-j X_C}$$

$$= \frac{1}{R} + \frac{1}{-j wC}$$

$$[\because X_C = \frac{1}{wC}]$$

$$\therefore I = \frac{1}{Z_{eq}} + j\omega C$$

$\frac{1}{Z_{eq}} = R - j \omega C$  yo mathi logo vade plus huxo

$$\frac{1}{Z_{eq}} = \frac{1}{R} + j\omega C$$

or, in adm. AD,

$$\frac{1}{Z_{eq}} = \frac{1}{R} + j\omega C$$

$$\text{or, } I = \frac{1}{Z_{eq}} + j\sqrt{2}\pi \times 1000 \times 0.1 \times 10^{-6}$$

$$= \frac{1}{300}$$

$$= 289.70 - j54.608$$

When,


bridge is balanced then,

$$Z_{AB} * Z_{DC} = Z_{BC} * Z_{AD}$$

$$\Rightarrow Z_{DC} = \frac{Z_{BC} * Z_{AD}}{Z_{AB}}$$

$$\Rightarrow Z_{DC} = \frac{300 (289.71 - 54.608j)}{-j795.77}$$
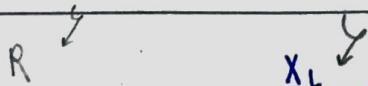
$$\therefore Z_{DC} = \underbrace{34.313}_{R} + j \underbrace{182.03}_{X_L}$$



As imag part has +ve value so there is inductor in ckt.

① When  $R \& L$  are in series

$$Z_{DC} = R + jX_L$$

so,

$$R = 31.313 \Omega$$

$$X_L = 182.03$$

$$X_L = \omega L$$

$$\text{or, } L = 182.03$$

$$2\pi \times 1000 \\ = 0.0289 \text{ H}$$

② When  $R \& L$  are in parallel

$$\frac{1}{Z_{DC}} = \frac{1}{R} + \frac{1}{jX_L}$$

$$\frac{1}{31.313 + 182.03j} = \frac{1}{R} + \frac{1}{jX_L}$$

$$\Rightarrow 0.001 - 0.005305j = \frac{1}{R} + \frac{1}{jX_L}$$

equating real & imag. part

$$1 = 0.001$$

R

$$\therefore R = 1000 \Omega$$

similarly,

$$-\textcircled{j} 0.005305 = 1 \\ \textcircled{j} X_L$$

$$\text{or, } \frac{1}{X_L} = 0.005305$$

$$\text{or, } 1 = \frac{1}{0.005305 \times 2\pi \times 1000}$$

$$\therefore L = 0.030H$$

Voltmeter-Ammeter method for measuring  
Resistance