

$$\epsilon_0 = \frac{k R_p}{R_p} * \epsilon_i$$

$$\therefore \epsilon_0 = k \epsilon_i \rightarrow (i)$$

$$\epsilon_0 = \frac{x_i}{x_t} \epsilon_i \rightarrow (ii)$$

$$\frac{\epsilon_0}{x_i} = \frac{\epsilon_i}{x_t} = \text{const.} \rightarrow (iii)$$

26th

Dec

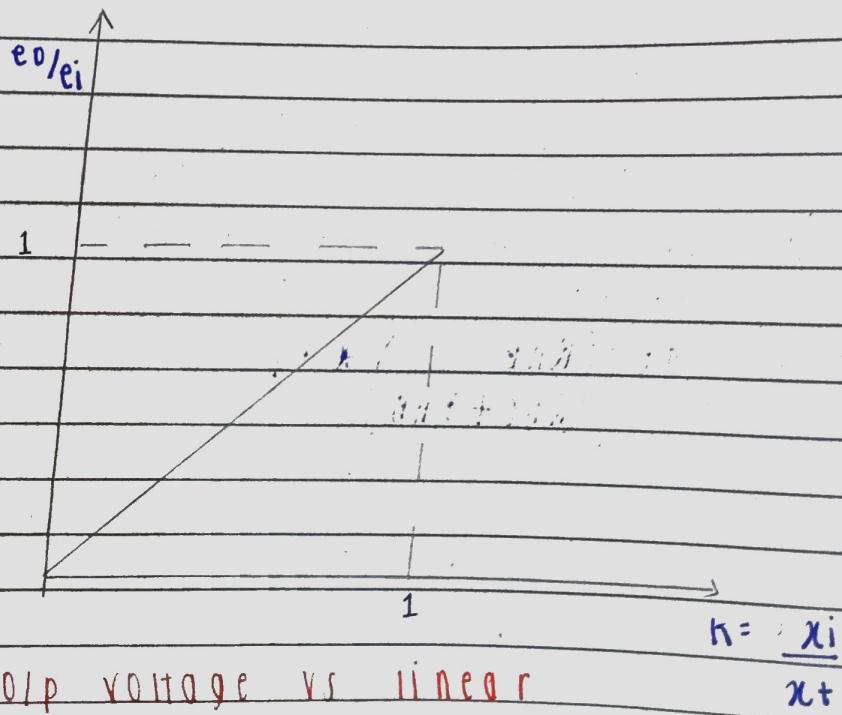


Fig: O/p voltage vs linear displacement in POT

$$k = \frac{x_i}{x_t}$$

From eqn (i), (ii) & (iii) we conclude that there exists a linear relⁿ betⁿ o/p voltage & i/p voltage.

So,

sensitivity \rightarrow constant

as shown in fig above

$$S = \frac{\text{mag. of o/p}}{\text{mag. of i/p}}$$

$$\therefore S = \frac{e_0}{x_i} = \frac{e_i}{\theta t} = K \text{ (constant)}$$

✓ ✓ ↗ (iv)

x_i θt

Eqn (i) - (iv) are also applicable to rotatory pot if we replace

$$x_i \rightarrow \theta i$$

$$\theta t \rightarrow \theta t$$

So,


eqn's becomes

$$e_0 = K e_i$$

$$e_0 = \frac{\theta i}{\theta t} e_i$$

$$\frac{e_0}{e_i} = \frac{\theta i}{\theta t} = k$$
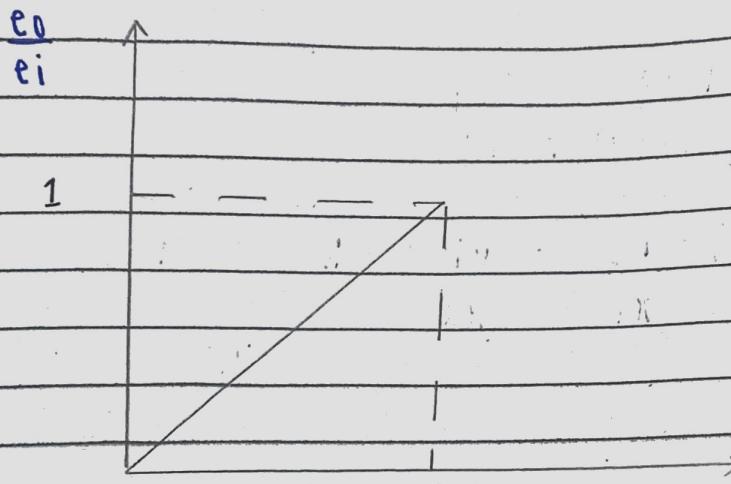
$$\frac{e_0}{e_i} = \frac{e_i}{\theta t} = \text{constant}$$



$$k = \frac{\theta i}{\theta t}$$

Fig: DIP VOLTAGE vs. ROTATIONAL
displacement in POT

LOADING EFFECT IN POT

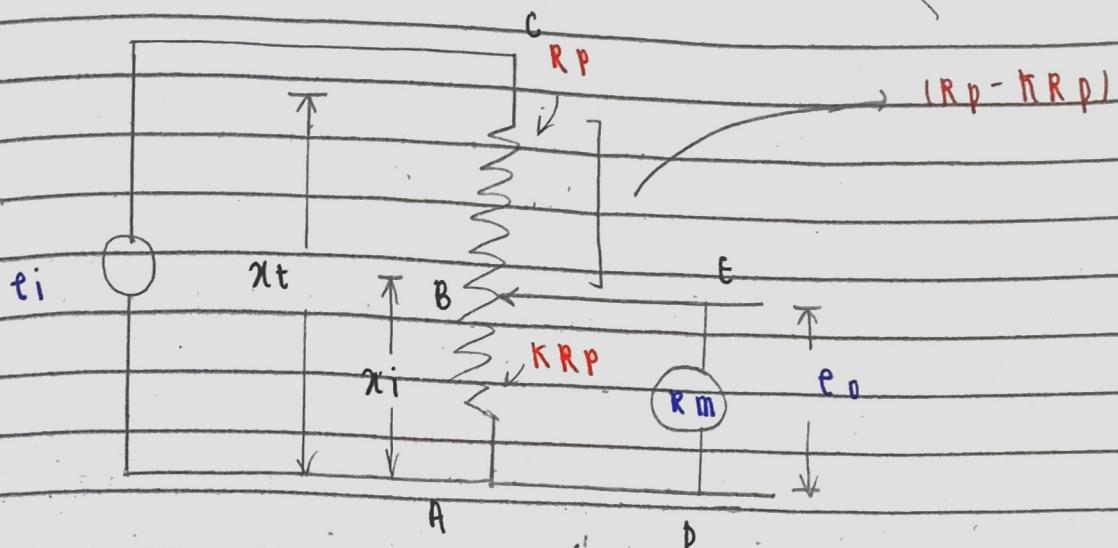


FIG: LOADED POT

If R of voltmeter $\rightarrow \infty$,

we get linear reln betⁿ
DIP & iip voltage.

given by

$$e_0 = K e_i = \frac{x_i}{x_t} e_i$$

L (i)

In actual practice, the iip or internal resistance (R_m) of voltmeter is \rightarrow finite.

So,

the reading indicated by voltmeter will always be \downarrow than value given by eqⁿ (i)

This effect is known as **loading effect**

∴

there exists an error known as
loading error

due to internal resistance / impedance of
o/p device.

Due to loading effect there exists a
non-linear reln betw o/p & i/p voltage

Here,

the resistance across R_{AB}

$$= K R_p // R_m$$

$$R_{AB} = \frac{K R_p R_m}{K R_p + R_m}$$

The o/p voltage due to loading effect
is given by

$$e_o = R_{AB} * e_i$$

$$(R_{AB} + R_{BC}) \text{ } \cancel{(R_p)}$$

Don't

forget


as

R_{AB} is not $K R_p *$

you quite add gara $R_p X$

gara varyana
aaaa

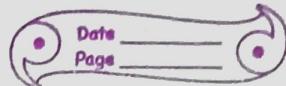As voltmeter jadesi equivalent R arnai
aaikayo. Taro Rp → same



so,

$$RBC = Rp - KR_p$$

thus,

$$e_0 = \frac{KR_p R_m}{KR_p + R_m} * ei$$

$$\frac{KR_p R_m}{KR_p + R_m} + \frac{(Rp - KR_p)}{KR_p + R_m}$$

$$= \frac{KR_p R_m}{KR_p + R_m} * ei$$

$$\frac{KR_p R_m + KR_p^2 - K^2 R_p^2 + R_m R_p - KR_p R_m}{KR_p + R_m} * ei$$

$$= \frac{KR_p R_m}{KR_p^2 - K^2 R_p^2 + R_p R_m} * ei$$

Dividing both by Rp Rm

$$= \frac{K}{\frac{R_p}{R_m} - \frac{K^2 R_p}{R_m} + 1} * ei$$

put Rm = α

Rp

$$= \frac{K}{\frac{K}{\alpha} - \frac{K^2}{\alpha} + 1} * ei$$

$$\therefore e_0 = \frac{\alpha \kappa}{\alpha + \kappa(1-\kappa)} \cdot e_i \quad \text{L (iii)}$$

If $R_m \rightarrow \infty$ then $\alpha \rightarrow \infty$

q

eqn (iii) becomes

$$e_0 = \kappa e_i$$

L (iv)

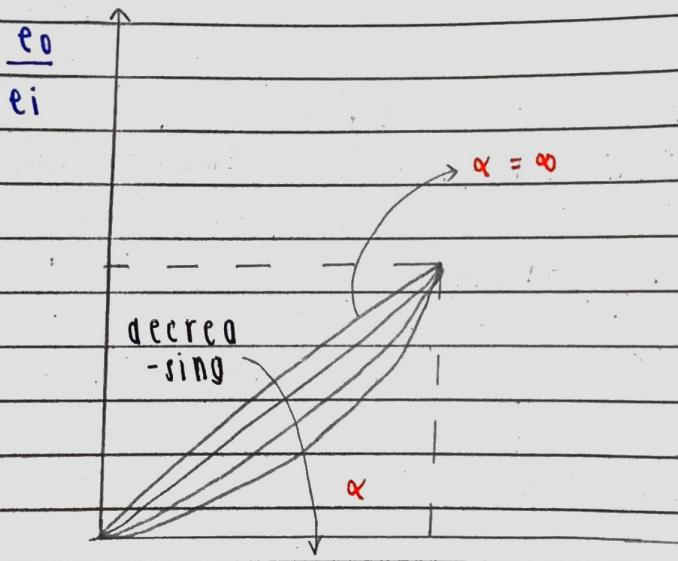


Fig (i)

$$\kappa = \frac{x_i}{x_i}$$

Eqn (iii) shows that there exists a non-linear relⁿ betn o/p & i/p due to the loading effect

graphically shown in fig (i)

loading error

① Relative error

② Absolute error

① Relative Error (Er)

$$Er = \frac{\text{o/p voltage w/o loading} - \text{o/p voltage w/ loading}}{\text{o/p voltage w/o loading}}$$

$$= \frac{\kappa e_i - \alpha \kappa e_i}{\kappa + \kappa(1-\kappa)} \\ = \frac{\kappa e_i}{\kappa + \kappa(1-\kappa)}$$

$$= \frac{1 - \alpha}{\alpha + \kappa(1-\kappa)}$$

$$= \frac{\alpha + \kappa(1-\kappa) - \alpha}{\alpha + \kappa(1-\kappa)}$$

$$Er = \frac{\kappa(1-\kappa)}{\alpha + \kappa(1-\kappa)} \quad \hookrightarrow (*)$$

F_r depends upon:

{ value of K

{ practical value of α

- To find K at which F_r is max. we have,

$$\frac{d(F_r)}{dK} = 0$$

$$\Rightarrow \frac{d}{dK} \left[\frac{K(1-K)}{\alpha + K(1-K)} \right] = 0$$

$$\Rightarrow \left[\frac{(\alpha + K(1-K))4(1-2K) - K(1-K)4(1-2K)}{(\alpha + K(1-K))^2} \right] = 0$$

$$\Rightarrow \alpha + K(1-K) - 2\alpha K - 2K^2(1-K) - K(1-K) + 2K^2(1-K) = 0$$

$$\Rightarrow \alpha - 2\alpha K = 0$$

$$\Rightarrow (1-2K)\alpha = 0$$

Y

$\alpha \neq 0$

$$\therefore \alpha = \frac{R_m}{R_p} \quad \text{if } R_m > R_p$$

betn 0 to 1
K Choi

$$\text{So, } 1 - 2K = 0$$

$$\therefore K = \frac{1}{2}$$

When $K = \frac{1}{2}$, E_r will be maximum

i.e. when the wiper is at mid-point of POT


NOW, let us plot the variation of E_r w.r.t. K for diff. value of α .

• FOR $K = 1$

K	E_r
0	0
0.1	0.0826
0.2	0.1379
0.3	0.1736
0.4	0.1935
0.5	0.2
0.6	0.1935
0.7	0.1736
0.8	0.1379
0.9	0.0826
1.0	0

• FOR $K = 0$

K	E_r
0	0
0.1	0.0089
0.2	0.0157
0.3	0.0206
0.4	0.0234
0.5	0.0244
0.6	0.0234
0.7	0.0206
0.8	0.0157
0.9	0.0089
1.0	0

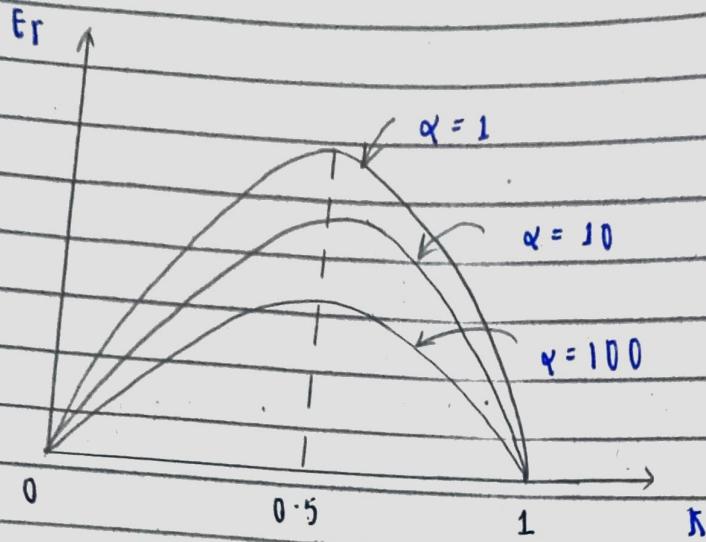

Fig(iii) VARIATION OF Fr W.R.T. K
ACC. TO α

From graph, we can see that

\downarrow
 • $Fr \downarrow$ w. \uparrow in α