

28th DEC

## TEST ON TRANSFORMER

- i) Polarity test
- ii) open circuit test / No load test
- iii) short circuit test


### ii) Polarity test

Dot convention are used to indicate the polarity.

- It gives the voltage polarity at the dotted terminal

→ I enter or leave doesn't matter

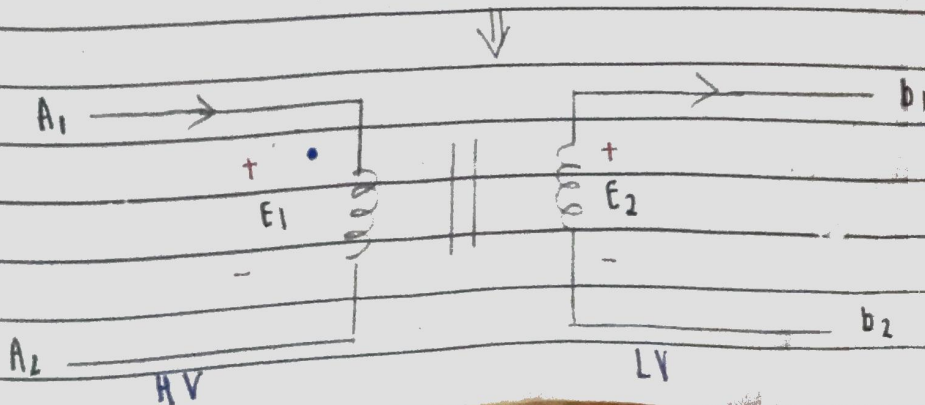- It is assumed that dotted terminal → +ve



**Note:** HV  $\rightarrow$  High voltage winding (capital)  $\rightarrow A_1, A_2$

LV  $\rightarrow$  low voltage winding (small)  $\rightarrow a_1, a_2$

Date \_\_\_\_\_  
Page \_\_\_\_\_

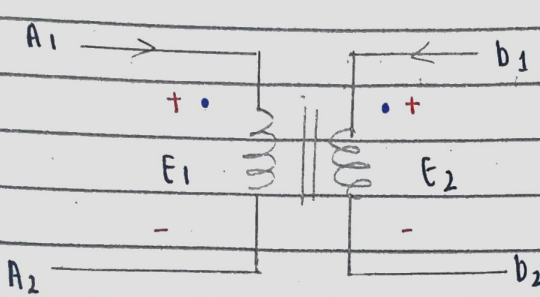


Fig: same polarity


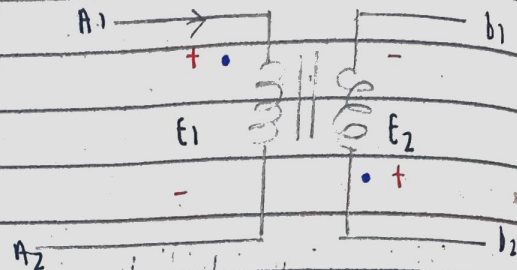


Fig: opposite polarity

## • circuit

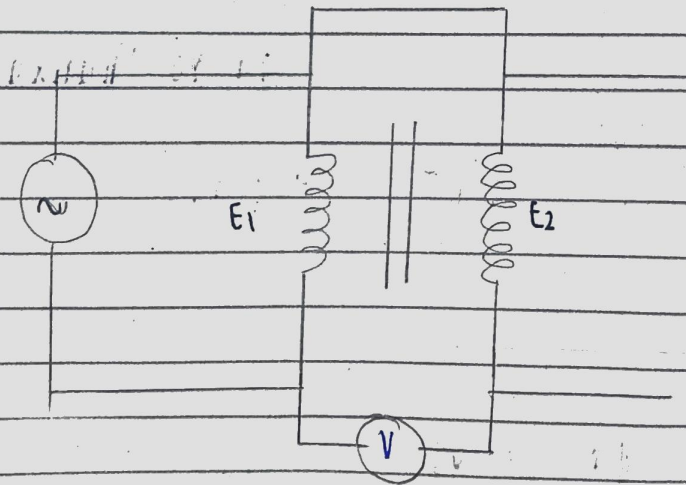

Two windings are connected in series across a voltmeter.

While,

one winding is excited by suitable voltage source as shown in fig

(a) CASE I :

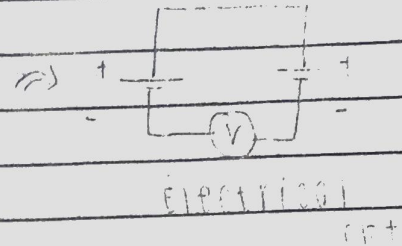
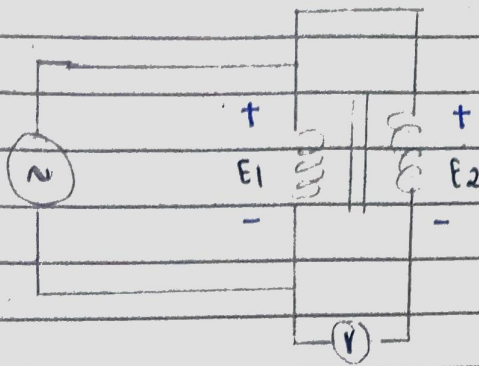


Fig: same polarity

• Voltmeter reading  $\rightarrow E_1 + E_2$

(b) CASE II :



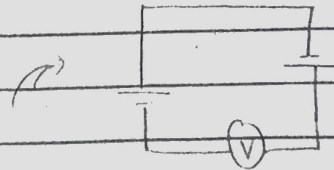


Fig: opp polarity

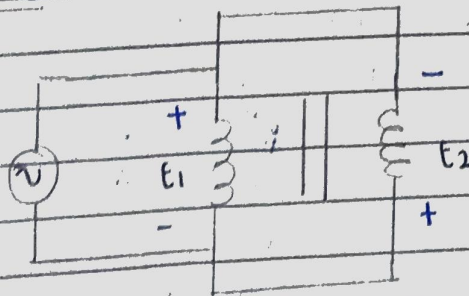• Voltmeter reading  $\rightarrow E_1 - E_2$



### iii) Open ckt Test / No load Test

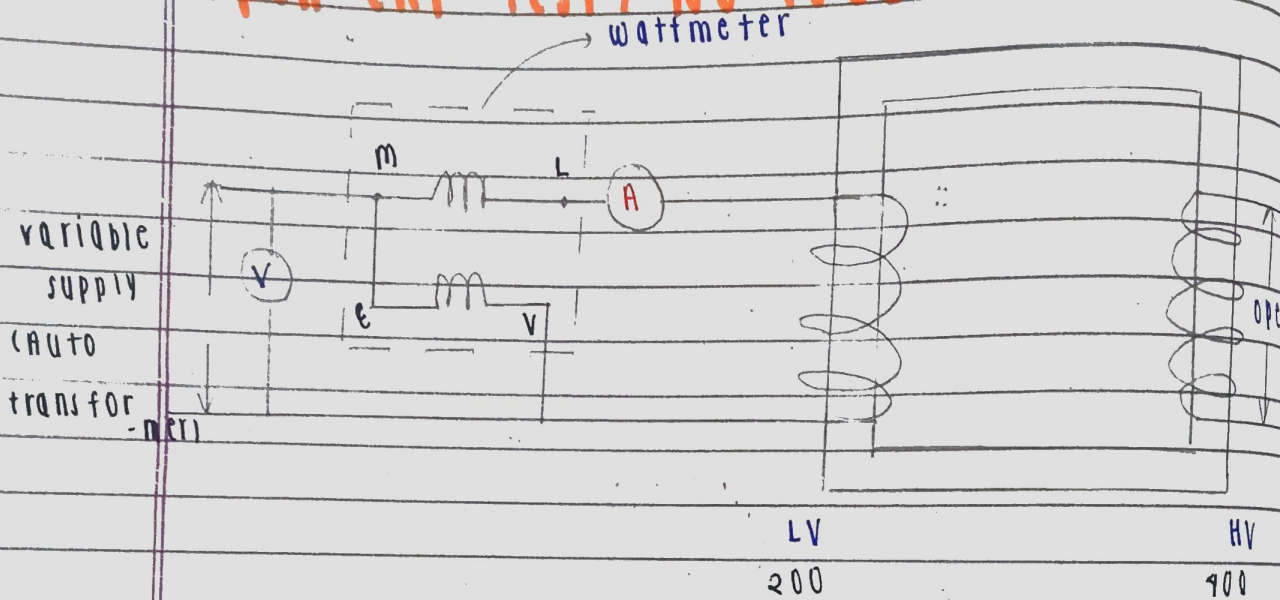

#### • Purpose :

Is to obtain :

- shunt branch parameter  
(magnetizing components)  
 $\downarrow$   
 $R_0$   $X_0$
- no load power loss  
(iron loss)
- no load power factor  
( $\cos \phi_0$ )

• **Note** : transformer no rating  $\frac{200}{400} \rightarrow 10 \text{ KO}$

200

↓

LV

400


↓

HV

400

↓

20 KO

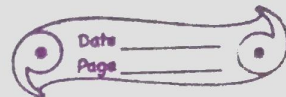

### • Procedure

usually,

- ammeter
  - voltmeter
  - wattmeter
- } are connected on low voltage side

to measure:

- no load current
- applied voltage
- power consumed.

The high voltage side  $\rightarrow$  kept open.

Gradually,

the supply voltage is varied till the voltmeter (V) shows the rated voltage of that side

i.e. 200V

let,

$W_0$  = wattmeter reading

$I_0$  = ammeter reading

$V_1$  = voltmeter reading

We know that,

$$W_0 = V_1 I_0 \cos \phi_0$$

$$\therefore \cos \phi_0 = \frac{W_0}{V_{ID}}$$

$$\phi_0 = \cos^{-1} \left( \frac{\omega_0}{V_{1J0}} \right)$$

$$I_e = I_o \cos \phi_o$$

$$I_m = I_0 \sin \phi_0$$

We know,

$$V = IR$$

$$\therefore R = \frac{V}{I}$$

$$R_D = \frac{V_1}{I_D}$$

$$X_0 = \frac{V_1}{I_m}$$

- Equivalent ckt of transformer on no load test

sabai in ref. to primary

50.

$$R_{01} = R_1 + \frac{R_2}{K^2}$$

20 lai 10. logne


$$v_{0ye} \div b_{ye} K^2$$

$$X_{01} = X_1 + \frac{X_2}{K^2}$$

10 to 20

VO VOYE X CY R.



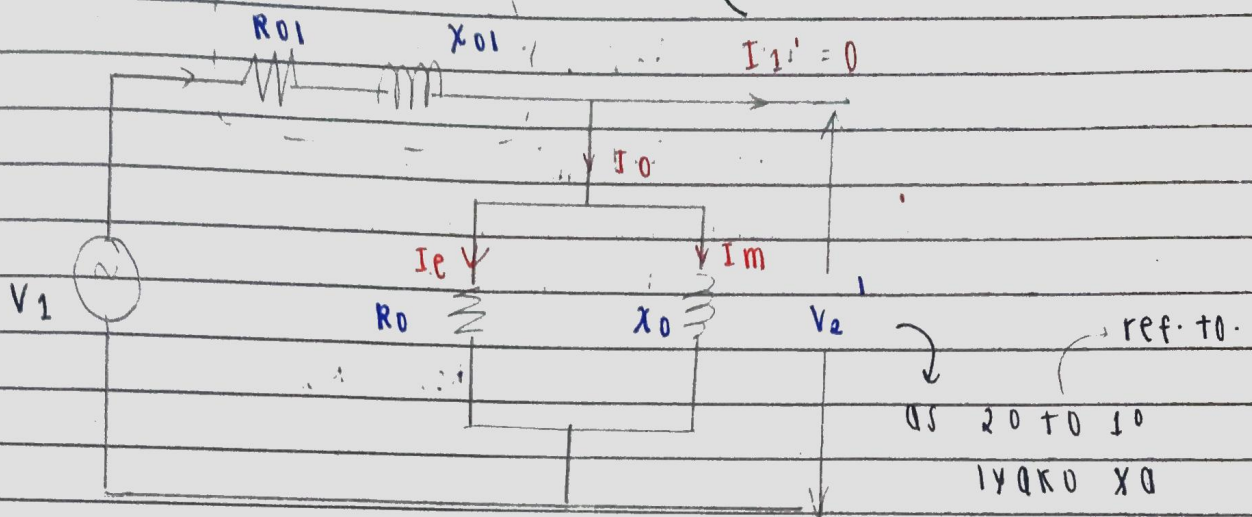

### Note:


400/200 ⇒ step down x<sub>0</sub>  
vane

all • ammeter  
• wattmeter  
• voltmeter } connected in 2<sup>o</sup> side

1<sup>o</sup> side remains open

ω<sub>0</sub>, I<sub>0</sub>, V<sub>1</sub> same

$$\omega_0 = V_2 I_0 \cos \phi_0$$

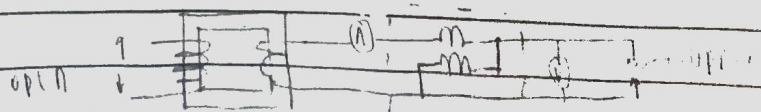

Watt in ref to 2<sup>o</sup> x 0 so

$$I_m' = I_0 \sin \phi_0$$

$$I_e' = I_0 \cos \phi_0$$

similarly,

$$R_0' = V_2 / I_e'$$

$$X_0' = V_2 / I_m'$$

40 actually no primary R0 no  
but its ref. to 2<sup>o</sup>

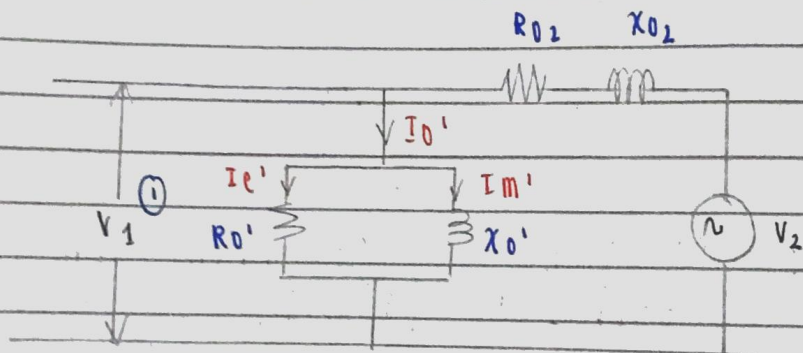


Fig: Equivalent ckt ref. to 2<sup>o</sup>